



UNIVERSITY EXAMINATIONS

SECOND SEMESTER 2023/2024 ACADEMIC YEAR

**SECOND YEAR EXAMINATION FOR THE DEGREE OF
BACHELOR OF SCIENCE IN (ICT)**

BICT 222: DIGITAL LOGICS

STREAM: R

TIME: 2 HRS

DAY: WEDNESDAY [2.30 – 4.30 P.M]

DATE: 10/04/2024

THIS QUESTION PAPER CONSISTS OF FOUR (4) PAGES

PLEASE DO NOT OPEN UNTIL THE INVIGILATOR SAYS SO.

INSTRUCTIONS: Section A is compulsory and has **30 marks**.

Attempt any **TWO** questions from Section B. Each question has **20 marks**.


Section A – 30 marks (Answer all questions)

QUESTION ONE (30 MARKS)

1. State and prove De Morgan's theorem. **(2 Marks)**
2. Differentiate between the following terms **(4 Marks)**
 - a. Combinational circuits and sequential circuits
 - b. Level triggered and edge triggered
3. Minimize the expression: $AB+AC'+BC$ using the theorem and properties of Boolean algebra. **(3 Marks)**
4. Using **(3 Marks)**
 - a. 1's complement, subtract (1000100-1010100).
 - b. Using 9's complement, subtract (3250 – 72532).
 - c. Using 10's complement, subtract (3250-72532).
5. Draw a logic gate that implements the following: **(4 Marks)**
 - a. $F = AB + C D' + B' C$
 - b. $F = (A + B) (B' + C) (C' + D + E)$
6. Perform the following operations: **(6 Marks)**
 - a. $100.1B_{16} - OFF.OD_{16}$ (Convert your answer to decimal)
 - b. $275_8 + 57_8$ (Convert your answer to hexadecimal)
 - c. Convert $(724.25)_8$ into octal
7. Draw a NAND gate realization of an edge triggered O flip flop and explain the operation of the flip flop. **(4 Marks)**
8.
 - a. Express the Boolean function $F = XY + X'Z$ in a product of max term form. **(2 Marks)**
 - b. Express the Boolean function $F = A + B'C$ in a sum of min terms. **(2 Marks)**

SECTION B – 40 MARKS (ANSWER ANY TWO QUESTIONS)

QUESTION TWO (20 MARKS)

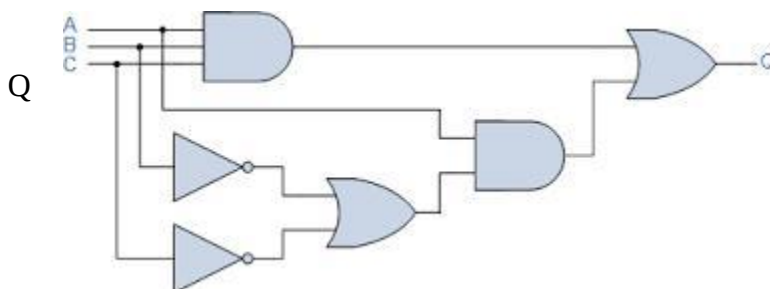

- a) The logic circuit below implements the function

(12 Marks)

- i. Generate the Boolean expression for the function Q
 - ii. Simplify the expression for Q
 - iii. Implement using NAND gates only
- b) Elucidate the following laws as espoused in digital systems **(8 Marks)**
- i. Associative Law
 - ii. Distributive Law
 - iii. Inverse Law
 - iv. Identity Law

QUESTION THREE (20 MARKS)


- a) Obtain a simplified expression for the K-map below and implement the simplified expression using logic gates **(6 Marks)**

Z C \ A	00	01	11	10
	00	01	11	10
00	0	0	1	1
01	1	0	1	1
11	0	0	0	0
10	1	1	1	1

b)

X B ₃ B ₂	B ₁ B ₀	01	11	10
	00	0	0	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

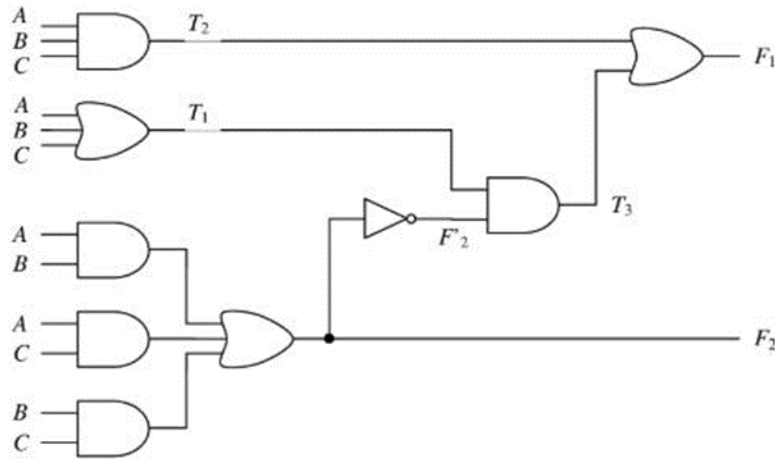- c) Prepare K-Map for the given function **(4 Marks)**
- $$f = AB + AC + B\bar{C}D$$
- d) Obtaining Boolean functions and Truth table from logic diagram. **(5 Marks)**



e) Draw a logic circuit to implement a half odder, obtain the truth table. (5 Marks)

QUESTION FOUR (20 MARKS)

a) Draw a logic gates that implements the following: (6 Marks)

- $F = AB + C D' + B' C$
- $F = (A + B) (B' + C) (C' + D + E)$

b) Simplify the following logic expression and draw the logic circuit for the simplified function

(4 Marks)

- $Y = (A+B)(A'+B')$
- $W = X.Y + X'.Y + X'Y'$

c) Design a 3 input majority function. The output is high if two or more inputs is high:

(6Marks)

- Show the truth table
- Derive the Boolean expression
- Implement using logic gates

d) With the aid of an illustration describe the two universal gates.

(4 Marks)

QUESTION FIVE (20 MARKS)

a) Describe the operation of a J-K flip flop. (6 Marks)

b) Using a J-K flip flop construct a 4-bit counter. (6 Marks)

c) Show the additional logic that need to be added to build a module 10 counter.

(4 Marks)

d) Describe propagation delay and the hazards associated with the delay.

(4 Marks)